

Assignment 1 – Cyclic Redundancy Check

Jorge Catarino (nº85028), Óscar Pimentel (nº80247)

Grupo 1 (P4) - ACA

Encoder - Our Approach

❏ Approach discussed in class - **Properties of the Remainder:**

- ❑ 64 XOR gates needed;
- ❑ 11 XOR propagation time delays in the worst case (r2);

❏ We took that basic solution and improved it by building a **Parallel implementation:**



- ❑ we displayed the basic approach on a table and we found common groups of operations, therefore reducing the gate count;
- ❑ we perform the operations in parallel, reducing the propagation time delays;

	r7	r6	r5	r4	r3	r2	r1	r0
a0				1		1	1	1
a1			1		1	1	1	1
a2		1		1	1	1	1	
a3			1		1		1	1
a4		1		1		1	1	1
a5			1	1	1		1	1
a6		1	1	1			1	1
a7		1	1	1			1	1
a8		1	1	1		1		1
a9		1	1	1	1	1	1	1
a10		1	1		1	1	1	1
a11		1					1	1
a12				1			1	1
a13			1			1	1	1
a14		1		1	1	1	1	1
a15							1	1

5	Porta 1	a8, a9
4	Porta 2	a6, a7
4	Porta 3	a2, a4
4	Porta 4	a3, a5
3	Porta 5	a0, a15
3	Porta 6	a10, a14
2	Porta 7	a11, a12
3	Porta 8	a1, a13
2	Porta 9	a1, a9

Encoder - Results

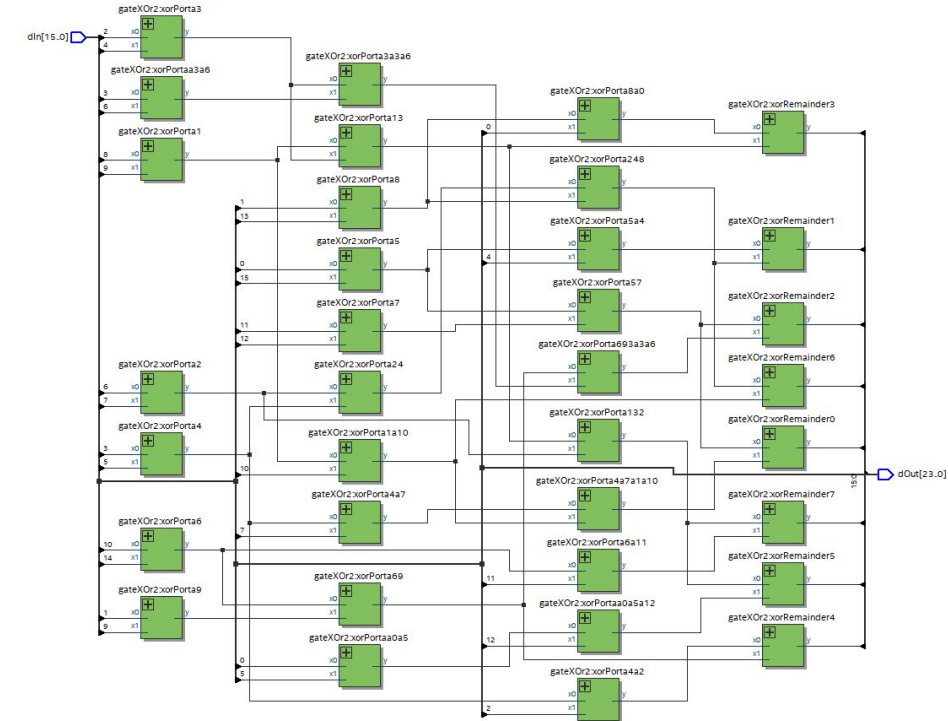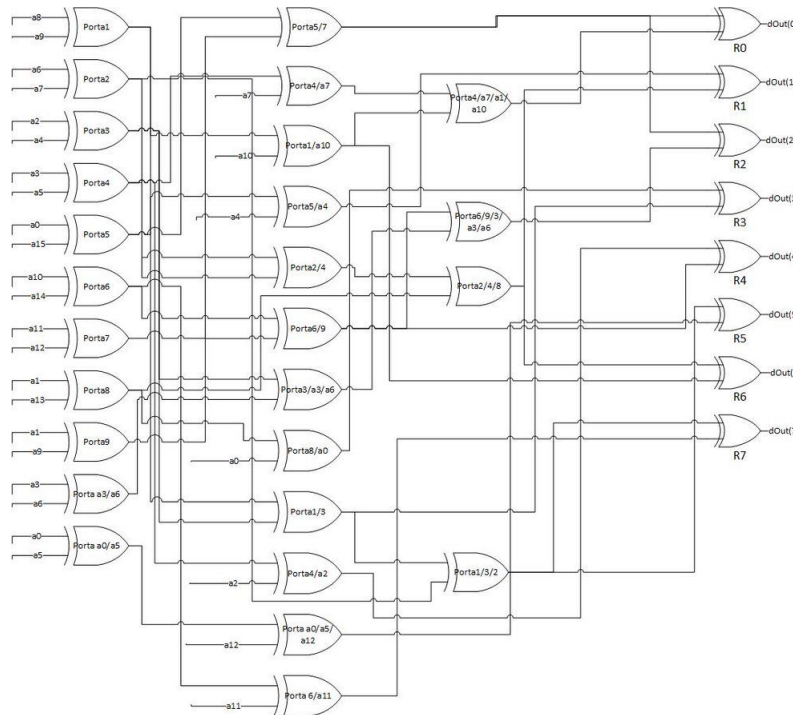- Improved worst case propagation delay -> 4 XOR propagation time delays (r0, r1, r2, r5, r6 and r7);
- Improved gate count -> 35 XOR gates;




Checker - Our Approach

❏ Approach discussed in class - **Division Algorithm**:


- ❑ When MSB is 0, shift left and bring the next bit down.
- ❑ When MSB is 1, XOR with divisor and shift left.
- ❑ With this algorithm, we can implement a **bit-serial solution**.

```
      0 0 0 0 1 0 1
1 0 0 1 1 | 1 0 1 1 0 0 1 0 0 0 0
      1 0 0 1 1
      -----
      0 0 1 0 1
        0 1 0 1 0
          1 0 1 0 1
            1 0 0 1 1
              0 0 1 0 0
```

 ❏ To implement this algorithm, we needed a shift register and a collection of modulo two adders (XOR). This module is called Linear Feedback Shift Register. With that we found two possible designs:



Checker - Results

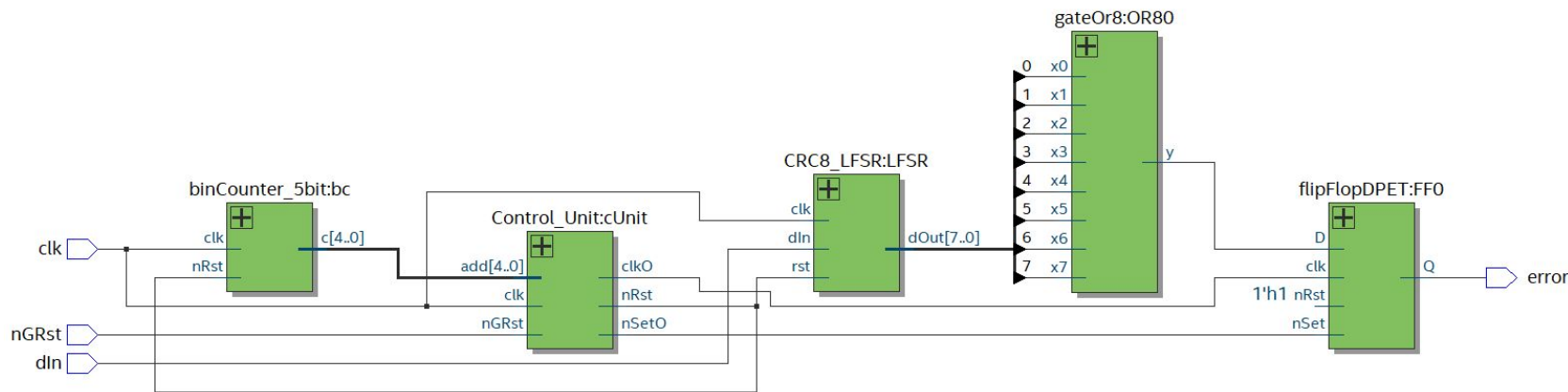



Implementation Cost:

- ❑ 1 LFSR
 - ❑ 8 Flip-Flop D, 5 XOR gates ;
- ❑ 1 5-bit Binary Counter
 - ❑ 5 Flip Flop D, 4 XOR gates, 3 AND gates ;
- ❑ 1 Control Unit ;
 - ❑ 4 NAND gates, 1 NOR gate
- ❑ 1 8-bit OR Gate;
- ❑ 1 Flip-Flop D;

Operation time:

- ❑ 26 clock cycles (24+2);

References

-  Culler, David. Lecture 26- LFSR, CRC's (and a little power). Fall 2004, <https://www-inst.eecs.berkeley.edu/~cs150/archives.html>. PowerPoint Presentation.
-  W. W. Peterson and D. T. Brown, "Cyclic Codes for Error Detection," in Proceedings of the IRE, vol. 49, no. 1, pp. 228-235, Jan. 1961, doi: 10.1109/JRPROC.1961.287814.